

# Nand2Tetris - The Elements of Computing Systems

Noam Nisan and Shimon Schocken

16th September 2013

## Abstract

The book's software suite:

**Simulators** *HardSimulator*, *CPUEmulator*, *VMEulator*.  
(supplied: build hardware platforms and execute programs)

**Translators** *Assembler*, *Jack Compiler*.  
(I built but also supplied: translate from high-level to low-level)

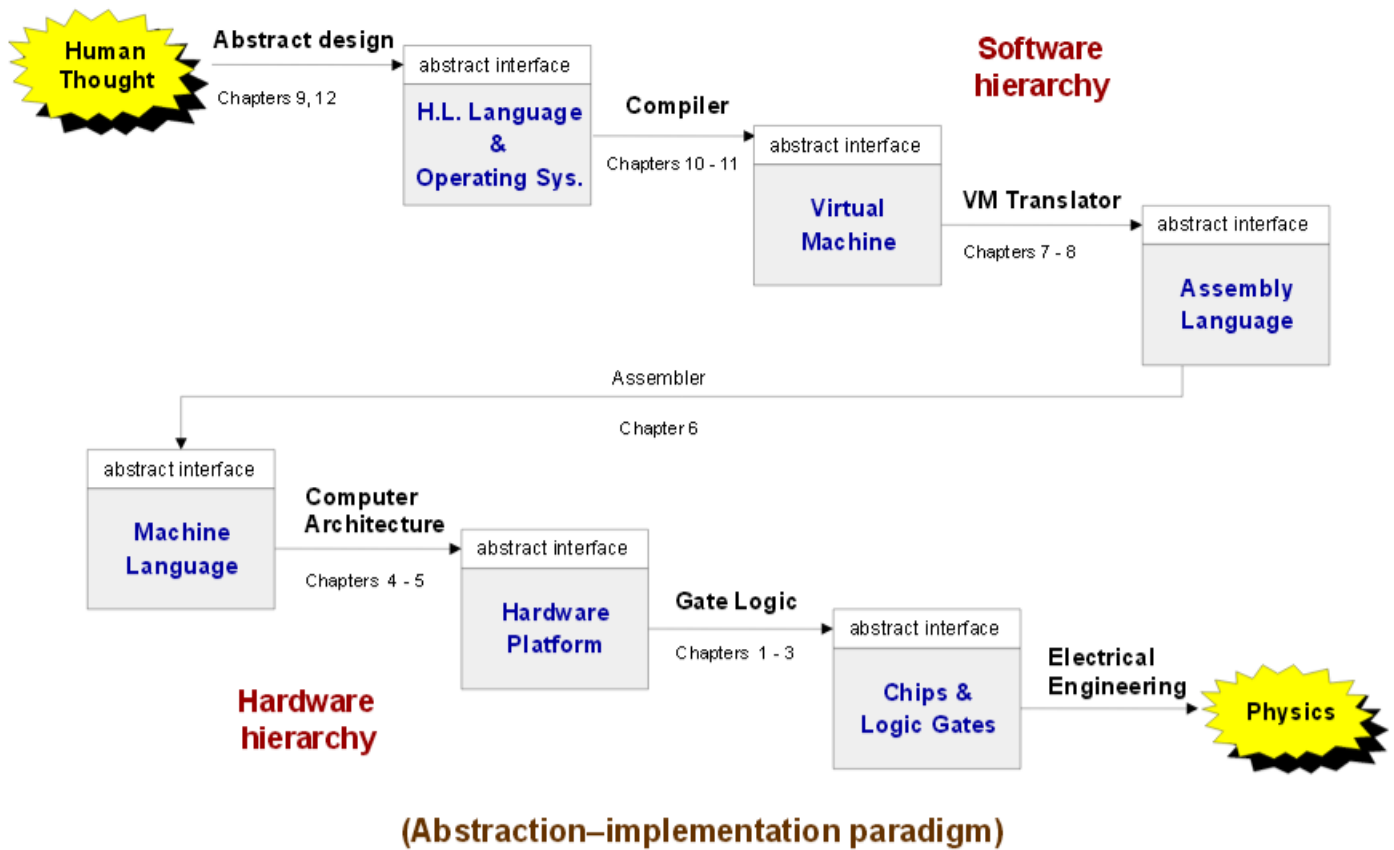


Figure 0.1: Course theme and structure.

# Contents

<b>1</b>	<b>Boolean Logic</b>	<b>3</b>
1.1	Background . . . . .	3
1.1.1	Boolean (Binary) Algebra [p8] . . . . .	3
1.1.2	Gate Logic [p11] . . . . .	4
1.1.3	Actual Hardware Construction [p13] . . . . .	4
1.1.4	(Virtual) Hardware Description Language, (V)HDL [p14] . . . . .	4
1.2	Specification . . . . .	5
1.2.1	The NAND Gate [p19] . . . . .	5
1.2.2	Basic Logic Gates [p19] . . . . .	5
1.2.3	Multi-Bit Versions of Basic Gates [p21] . . . . .	6
1.2.4	Multi-Way Versions of Basic Gates [p23] . . . . .	7
1.3	Implementation [p25] . . . . .	8
1.4	Project [p27] . . . . .	9
1.5	Perspective [p26] . . . . .	9
<b>2</b>	<b>Boolean Arithmetic [p29]</b>	<b>10</b>
2.1	Background [p30] . . . . .	10
2.1.1	Binary numbers and addition [p30] . . . . .	10
2.1.2	Signed Binary Numbers [p31] . . . . .	10
2.2	Specification [p32] . . . . .	11
2.2.1	Adders . . . . .	12
2.2.2	The Arithmetic Logic Unit (ALU) [p35] . . . . .	12
<b>3</b>	<b>Sequential Logic [p41]</b>	<b>15</b>
3.1	Background [p42] . . . . .	15
3.1.1	Sequential VS. Combinational Logic . . . . .	15
3.1.2	Memory [p42] . . . . .	15
3.2	Specification [p47] . . . . .	19
3.3	Implementation [p50] . . . . .	19
3.4	Perspective [p52] . . . . .	19
<b>4</b>	<b>Machine Language [p57]</b>	<b>20</b>

# 1 Boolean Logic

## 1.1 Background

### 1.1.1 Boolean (Binary) Algebra [p8]

**Boolean functions** operate on binary inputs, returning binary outputs; use *truth tables* to represent functions.

Notation	Boolean Expression
$x \cdot y = xy$	$x$ AND $y$
$x + y$	$x$ OR $y$
$\bar{x}$	NOT $x$

Table 1.1: Boolean expressions created from the Boolean operators “AND”, “OR” and “NOT”.

### Boolean Expressions

**Canonical Representation** *Every Boolean function can be expressed using one Boolean expression.*

Method: (see E1.1)

1. Mark every row for which the function has value 1.
2. AND together the *literals* (the variable itself or it’s negation) for each of these rows.
3. OR these terms.

**Corollary 1.1.** *Every Boolean function can be expressed using three Boolean operators AND, OR, NOT.*

*Note.* The number of Boolean functions that can be defined over  $n$  binary variable is  $2^{2^n}$ .

**Example (E1.1).** Consider the Boolean Expression  $f(x, y, z) = (x + y) \cdot \bar{z}$ .

$x$	$y$	$z$	$f(x, y, z)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

*Canonical Form:*  $f(x, y, z) = \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy\bar{z}$ . Observe can be factored further, yet remains clearer regarding the truth table in this form.

*Remark.* The NAND function can construct each one of the AND, OR, and NOT operations, and since these three operations can express every Boolean expression it follows:

**Theorem 1.2.** *Every Boolean function can be constructed from NAND alone.*

Operation	Construction from NAND
AND	$\text{Nand}(\text{Nand}(x, y), \text{Nand}(x, y))$
OR	$\text{Nand}(\text{Nand}(x, x), \text{Nand}(y, y))$
NOT	$\text{Nand}(x, x)$
NOR	“We’ve already created NOT and OR.” $\text{NOT}(\text{OR}(x, y))$
XOR	Similarly: $\text{OR}(\text{AND}(x, \text{NOT}(y)), \text{AND}(\text{NOT}(x), y))$

## 1.1.2 Gate Logic [p11]

**Chip/Gate** A physical device that implements a Boolean function.

If a Boolean function  $f$  operates on  $n$  variables and returns  $m$  binary results, the gate that implements  $f$  will have  $n$  input pins and  $m$  output pins.

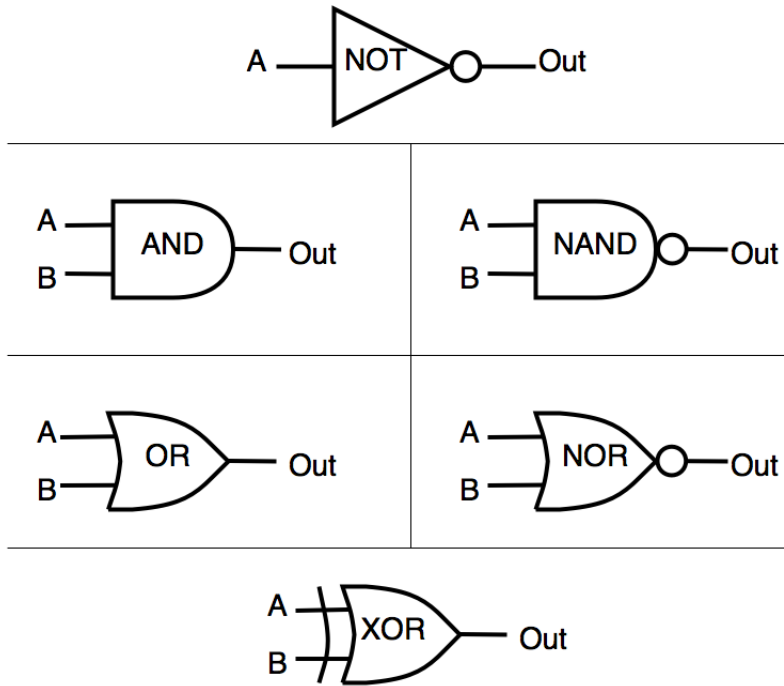
 
 
**Gate interface**

Figure 1.1: Left: Standard logic gate symbols. Right: **WHAT** a three-way AND gate is doing, and **HOW** it operates. Observe *the gate interface is unique, whilst there exists many different implementations*. The art of logic design is: *Given a gate specification, find an efficient way to implement it using other gates that were already implemented*.

## 1.1.3 Actual Hardware Construction [p13]

Gets Messy!

## 1.1.4 (Virtual) Hardware Description Language, (V)HDL [p14]

- Hardware designers specify the chip's structure by writing an *HDL program* (c.f. a programming language).
- The designs are then subjected to rigorous testing using a *hardware simulator* (c.f. a compiler).

**Example** (E1.2).

 


Figure 1.2: Designing a XOR gate using HDL, with test and output file.

## 1.2 Specification

### 1.2.1 The NAND Gate [p19]

<i>a</i>	<i>b</i>	NAND ( <i>a</i> , <i>b</i> )
0	0	1
0	1	1
1	0	1
1	1	0

*Remark.* Throughout this course, we use *chip API boxes* to specify chips:





```

Chip name: Nand
Inputs:    a, b
Outputs:   out
Function:  If a=b=1 then out=0 else out=1
Comment:   This gate is considered primitive and thus there is
               no need to implement it.

```

Figure 1.3: *Chip API box* for a NAND chip.

### 1.2.2 Basic Logic Gates [p19]

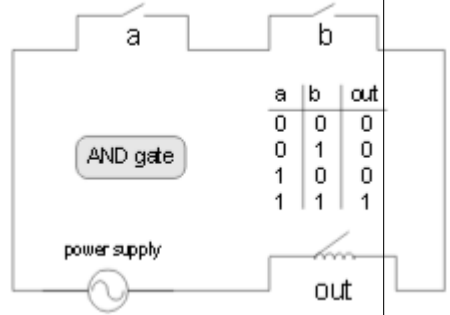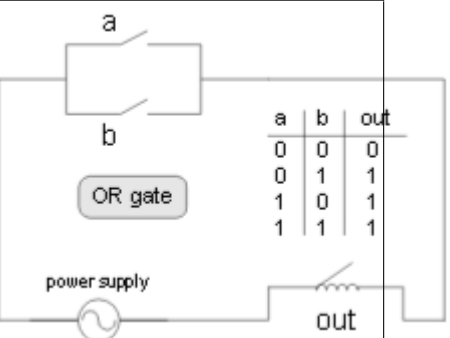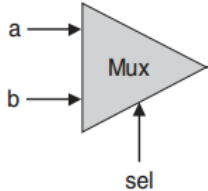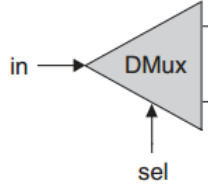Gate	Chip API Box	Circuit Implementations															
NOT	<b>Chip name:</b> Not <b>Inputs:</b> in <b>Outputs:</b> out <b>Function:</b> If in=0 then out=1 else out=0.																
AND	<b>Chip name:</b> And <b>Inputs:</b> a, b <b>Outputs:</b> out <b>Function:</b> If a=b=1 then out=1 else out=0	 <table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>out</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	out	0	0	0	0	1	0	1	0	0	1	1	1
a	b	out															
0	0	0															
0	1	0															
1	0	0															
1	1	1															
OR	<b>Chip name:</b> Or <b>Inputs:</b> a, b <b>Outputs:</b> out <b>Function:</b> If a=b=0 then out=0 else out=1	 <table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>out</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	out	0	0	0	0	1	1	1	0	1	1	1	1
a	b	out															
0	0	0															
0	1	1															
1	0	1															
1	1	1															
XOR	<b>Chip name:</b> Xor <b>Inputs:</b> a, b <b>Outputs:</b> out <b>Function:</b> If a≠b then out=1 else out=0.																
MULTIPLEXOR	 <b>Chip name:</b> Mux <b>Inputs:</b> a, b, sel <b>Outputs:</b> out <b>Function:</b> If sel=0 then out=a else out=b.																
DEMULTIPLEXOR	 <b>Chip name:</b> DMux <b>Inputs:</b> in, sel <b>Outputs:</b> a, b <b>Function:</b> If sel=0 then {a=in, b=0} else {a=0, b=in}.																

### 1.2.3 Multi-Bit Versions of Basic Gates [p21]

- Computer hardware is typically designed to operate on multi-bit arrays called *buses*.
- When referring to individual bits in a bus (suppose we are dealing with a 16-bit bus named `data`), it is common to use the array syntax `data[0]`, `data[1]`, ..., `data[15]`.

*Remark* (Backwards Conveyor Belt). Arrays are specified from right-to-left in the HDL used.

<i>n</i> -bit Gate	Chip API Box (16-bit gate)
MULTI-BIT NOT	<b>Chip name:</b> Not16 <b>Inputs:</b> in[16] // a 16-bit pin <b>Outputs:</b> out[16] <b>Function:</b> For i=0..15 out[i]=Not(in[i]).
MULTI-BIT AND	<b>Chip name:</b> And16 <b>Inputs:</b> a[16], b[16] <b>Outputs:</b> out[16] <b>Function:</b> For i=0..15 out[i]=And(a[i],b[i]).
MULTI-BIT OR	<b>Chip name:</b> Or16 <b>Inputs:</b> a[16], b[16] <b>Outputs:</b> out[16] <b>Function:</b> For i=0..15 out[i]=Or(a[i],b[i]).
MULTI-BIT MULTIPLEXOR	<b>Chip name:</b> Mux16 <b>Inputs:</b> a[16], b[16], sel <b>Outputs:</b> out[16] <b>Function:</b> If sel=0 then for i=0..15 out[i]=a[i] else for i=0..15 out[i]=b[i].

#### 1.2.4 Multi-Way Versions of Basic Gates [p23]

- **Idea:** Evaluating more than 2 inputs.

<i>n</i> -way Gate	Chip API Box (8-way gate)
MULTI-BIT OR	<p><b>Chip name:</b> Or8Way</p> <p><b>Inputs:</b> in[8]</p> <p><b>Outputs:</b> out</p> <p><b>Function:</b> out=Or(in[0],in[1],...,in[7]).</p>
MULTI-WAY/MULTI-BIT MULTIPLEXOR	<p>An <math>m</math>-way, <math>n</math>-bit multiplexor selects one of <math>m</math> <math>n</math>-bit input buses and outputs it to a single <math>n</math>-bit output bus. The selection is specified by a set of <math>k = \log_2 m</math> control bits.</p> <p><b>Chip name:</b> Mux4Way16</p> <p><b>Inputs:</b> a[16], b[16], c[16], d[16], sel[2]</p> <p><b>Outputs:</b> out[16]</p> <p><b>Function:</b> If sel=00 then out=a else if sel=01 then out=b else if sel=10 then out=c else if sel=11 then out=d</p> <p><b>Comment:</b> The assignment operations mentioned above are all 16-bit. For example, "out=a" means "for i=0..15 out[i]=a[i]".</p> <p><b>Chip name:</b> Mux8Way16</p> <p><b>Inputs:</b> a[16],b[16],c[16],d[16],e[16],f[16],g[16],h[16], sel[3]</p> <p><b>Outputs:</b> out[16]</p> <p><b>Function:</b> If sel=000 then out=a else if sel=001 then out=b else if sel=010 out=c ... else if sel=111 then out=h</p> <p><b>Comment:</b> The assignment operations mentioned above are all 16-bit. For example, "out=a" means "for i=0..15 out[i]=a[i]".</p>
MULTI-WAY/MULTI-BIT DEMULTIPLEXOR	<p>An <math>m</math>-way <math>n</math>-bit demultiplexor channels a single <math>n</math>-bit input into one of <math>m</math> possible <math>n</math>-bit outputs. The selection is specified by a set of <math>k</math> control bits, where <math>k = \log_2 m</math>.</p> <p><b>Chip name:</b> DMux4Way</p> <p><b>Inputs:</b> in, sel[2]</p> <p><b>Outputs:</b> a, b, c, d</p> <p><b>Function:</b> If sel=00 then {a=in, b=c=d=0} else if sel=01 then {b=in, a=c=d=0} else if sel=10 then {c=in, a=b=d=0} else if sel=11 then {d=in, a=b=c=0}.</p> <p><b>Chip name:</b> DMux8Way</p> <p><b>Inputs:</b> in, sel[3]</p> <p><b>Outputs:</b> a, b, c, d, e, f, g, h</p> <p><b>Function:</b> If sel=000 then {a=in, b=c=d=e=f=g=h=0} else if sel=001 then {b=in, a=c=d=e=f=g=h=0} else if sel=010 ... else if sel=111 then {h=in, a=b=c=d=e=f=g=0}.</p>

### 1.3 Implementation [p25]

**Primitive Gates** provide a set of elementary building blocks from which everything else can be built.

*Remark* (C.f. Axioms in mathematics). We use NAND as our basic building block, yet other ones are possible (e.g. NOR, or a combination of AND,OR and NOT); **just as all theorems in geometry can be founded on different sets of axioms.**



**1.4 Project [p27]**

**1.5 Perspective [p26]**

## 2 Boolean Arithmetic [p29]

### 2.1 Background [p30]

#### 2.1.1 Binary numbers and addition [p30]

When we press the keyboard keys labelled **1**, **9** and **Enter**, the equivalent 32-bit binary code (if we are working on a 32-bit machine) **00000000000000000000000010011** ends up in the register of the computer's memory.

**LSB (Least Significant Bits)** the right-most digits of a binary number.

**MSB (Most Significant Bits)** the left-most digits of a binary number.

$$\begin{array}{r}
 \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{1} \\
 \hline
 \phantom{0} 1 \text{ } 0 \text{ } 0 \text{ } 1 \\
 \phantom{0} 0 \text{ } 1 \text{ } 0 \text{ } 1 \\
 \hline
 \textcolor{red}{0} \text{ } 1 \text{ } 1 \text{ } 1 \text{ } 0 \\
 \text{no overflow}
 \end{array}
 +
 \begin{array}{r}
 \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \\
 \hline
 \phantom{0} 1 \text{ } 0 \text{ } 1 \text{ } 1 \\
 \phantom{0} 0 \text{ } 1 \text{ } 1 \text{ } 1 \\
 \hline
 \textcolor{red}{1} \text{ } 0 \text{ } 0 \text{ } 1 \text{ } 0 \\
 \text{overflow}
 \end{array}$$

Figure 2.1: *Add digit by digit from right to left.* Observe, computer hardware for binary addition of 2  $n$ -bit numbers can be built from logic gates designed to calculate the **sum of 3 bits** (pair of bits plus carry bit) - hence the **full adder**.

#### 2.1.2 Signed Binary Numbers [p31]

A binary system with  $n$  digits can generate a set of  $2^n$  different bit patterns; hence if we need to represent positive and negative numbers, we split these arrangements into 2 equal subsets (one for the positive numbers, the other for the negative numbers).

**Definition 2.1.** The *2's (or radix) complement method* of a number  $x$  is

$$\bar{x} = \begin{cases} 2^n - x & \text{if } x \neq 0 \\ 0 & \text{otherwise} \end{cases}$$

This is equivalent to *inverting each digit and adding 1*.

0	0000		
1	0001	1111	-1
2	0010	1110	-2
3	0011	1101	-3
4	0100	1100	-4
5	0101	1011	-5
6	0110	1010	-6
7	0111	1001	-7
		1000	-8

$$2 - 5 = 2 + (-5) =$$

0	0	1	0
+	1	0	1
<hr/>			
1	1	0	1
			= -3

Figure 2.2: 2's complement representation of signed number in a 4-bit binary system. Observe the total number of numbers represent is  $2^n$ , with  $2^{n-1}$  is each subset. Also, the addition of a number an its inverse is 0000 (e.g.  $1 + (-1) = 0001 + 1111 = (1)0000$ , where the leading 1 is omitted because we're working in a 4-bit binary system. This representation of negative numbers makes subtraction very easy - as shown right. We conclude that all basic arithmetic and logical operators can be perform by a single chip (**ALU**).

**Example (E2.1).**

**ALU (Arithmetic Logical Unit)** the centrepiece chip or the CPU (which is the centrepiece of a computer) that executes all arithmetic and logical operations.

*Remark.* All positive number begin with 0, and all negative numbers begin with 1.

## 2.2 Specification [p32]

One such ALU is the *adder* chip.

## 2.2.1 Adders

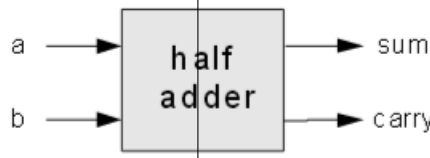
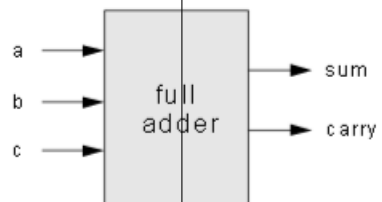

Adder	Implementation																																													
<p><i>Half-adder</i>: designed to add 2 bits. Based on the XOR and AND gates</p>	<table><tr><th>a</th><th>b</th><th>sum</th><th>carry</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr></table> 	a	b	sum	carry	0	0	0	0	0	1	1	0	1	0	1	0	1	1	0	1																									
a	b	sum	carry																																											
0	0	0	0																																											
0	1	1	0																																											
1	0	1	0																																											
1	1	0	1																																											
<p><i>Full-adder</i>: designed to add 3 bits. Can be based on half-adder gates.</p>	<table><tr><th>a</th><th>b</th><th>c</th><th>sum</th><th>carry</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> 	a	b	c	sum	carry	0	0	0	0	0	0	0	1	1	0	0	1	0	1	0	0	1	1	0	1	1	0	0	1	0	1	0	1	0	1	1	1	0	0	1	1	1	1	1	1
a	b	c	sum	carry																																										
0	0	0	0	0																																										
0	0	1	1	0																																										
0	1	0	1	0																																										
0	1	1	0	1																																										
1	0	0	1	0																																										
1	0	1	0	1																																										
1	1	0	0	1																																										
1	1	1	1	1																																										
<p><i>Multi-bit Adder</i>: designed to add two <math>n</math>-bit numbers (<math>n \in \{16, 32, 64, \dots\}</math>). Array of full-adder gates.</p>	 <table><tr><td>...</td><td>1</td><td>0</td><td>1</td><td>1</td><td>a</td></tr><tr><td></td><td></td><td></td><td></td><td></td><td>+</td></tr><tr><td>...</td><td>0</td><td>0</td><td>1</td><td>0</td><td>b</td></tr><tr><td colspan="6"><hr/></td></tr><tr><td>...</td><td>1</td><td>1</td><td>0</td><td>1</td><td>out</td></tr></table> <p>16-bit adder</p>	...	1	0	1	1	a						+	...	0	0	1	0	b	<hr/>						...	1	1	0	1	out															
...	1	0	1	1	a																																									
					+																																									
...	0	0	1	0	b																																									
<hr/>																																														
...	1	1	0	1	out																																									

Table 2.1: Hierarchy of three adders.

*Incrementer*: it is convenient to have a chip dedicated to adding the constant 1 to a given number (e.g. for calculating negative numbers).


## 2.2.2 The Arithmetic Logic Unit (ALU) [p35]

This subsection describes an ALU that will become the centerpiece of our computer platform *Hack*. The Hack ALU computes a fixed set of function  $out = f_i(x, y)$  where  $x, y$  are two 16-bit inputs,  $out$  a 16-bit output and  $f_i$  is an arithmetic or logical function selected from a fixed set of eighteen possible functions:

These bits instruct how to preset the $x$ input		These bits instruct how to preset the $y$ input		This bit selects between + / And	This bit inst. how to postset out	Resulting ALU output
$zx$	$nx$	$zy$	$ny$	$f$	$no$	$out=$
if $zx$ then $x=0$	if $nx$ then $x=1x$	if $zy$ then $y=0$	if $ny$ then $y=1y$	if $f$ then $out=x+y$ else $out=x\&y$	if $no$ then $out=lout$	$f(x,y)=$
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	$x$
1	1	0	0	0	0	$y$
0	0	1	1	0	1	$1x$
1	1	0	0	0	1	$1y$
0	0	1	1	1	1	$-x$
1	1	0	0	1	1	$-y$
0	1	1	1	1	1	$x+1$
1	1	0	1	1	1	$y+1$
0	0	1	1	1	0	$x-1$
1	1	0	0	1	0	$y-1$
0	0	0	0	1	0	$x+y$
0	1	0	0	1	1	$x-y$
0	0	0	1	1	1	$y-x$
0	0	0	0	0	0	$x\&y$
0	1	0	1	0	1	$x y$

Figure 2.3: The ALU truth table working with **16-bit** inputs/output (so if  $zy = 1$ ,  $y$  would zeroed  $y = (000...00)_2$  and in general  $0 = (000...00)_2$ ,  $1 = (111...11)_2$ ; note !=Not, &=And and |=Or (performed **bit-wise**). We designed the ALU by defining which functions were desired and worked backwards to figure out how  $x, y$  and  $out$  can be manipulated by binary operations to achieve these results. We have included the 6 control bits, each using a straightforward binary operation.

 *Remark.* We instruct the ALU which function to compute by setting six input bits, called *control bits*; hence we have  $2^6 = 64$  different functions (the function can either be included or not). 18 are of interest to us.



```

Chip name: ALU
Inputs:   x[16], y[16],      // Two 16-bit data inputs
          zx,                // Zero the x input
          nx,                // Negate the x input
          zy,                // Zero the y input
          ny,                // Negate the y input
          f,                 // Function code: 1 for Add, 0 for And
          no,                // Negate the out output
Outputs:  out[16],          // 16-bit output
          zr,                // True iff out=0
          ng,                // True iff out<0
Function: if zx then x = 0    // 16-bit zero constant
          if nx then x = 1x   // Bit-wise negation
          if zy then y = 0    // 16-bit zero constant
          if ny then y = 1y   // Bit-wise negation
          if f then out = x + y // Integer 2's complement addition
            else out = x & y // Bit-wise And
          if no then out = 1out // Bit-wise negation
          if out=0 then zr = 1 else zr = 0 // 16-bit eq. comparison
          if out<0 then ng = 1 else ng = 0 // 16-bit neg. comparison
Comment:  Overflow is neither detected nor handled.

```

Figure 2.4: ALU specification (not particular efficient; we have chose to specify an ALU hardware with limited functionality and implement as many operations as possible in software - operating system).

*Note.* The overall functionality of the hardware/software platform is delivered jointly by the **ALU** and the **operating system**.

### 3 Sequential Logic [p41]

#### 3.1 Background [p42]

##### 3.1.1 Sequential VS. Combinational Logic


All the chips discussed and built so far are combinational chips:

**Combinational devices** operate on data only; compute functions that depend solely on *combinations of their values*. This type of chip cannot store and recall values.

**Sequential devices** operate on data and a clock signal; can be *state-aware* and provide storage and synchronisation services.

The low-level behaviour of sequential gates is **tricky**; although

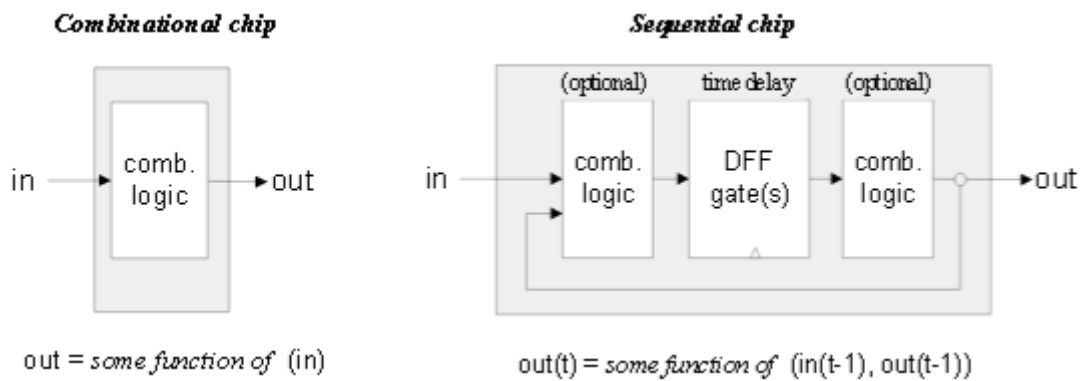**Theorem 3.1.** *Every sequential chip can be based upon the “data flip flop” or DFF sequential gate.*



##### 3.1.2 Memory [p42]

The act of “remembering something” is *time-dependent* (you remember now what has been committed to memory before). So for chip to “remember”, we require s means for representing the progression of time.

##### Hierarchy of memory chips:

- Flip-flop gates.
- Binary cells.
- Registers.
- RAM.

**The Clock** Most computers have a master clock that delivers a continuous train of alternating signals between two phases labelled “0” and “1”. The elapsed time between “0” and “1” is the *cycle*, and each clock cycle represent on discrete time unit.


**Flip-Flops** We consider a variant of a flip-flop called the *data flip-flop*, whose interface consists of a single-bit data input/output, and a *clock* (continuously changing) according to the master clock’s signal:  $out(t) = in(t-1)$  where  $in/out$  are the input/output values and  $t$  is the current clock cycle.




**Chip name:** DFF  
**Inputs:** in  
**Outputs:** out  
**Function:**  $out(t) = in(t-1)$   
**Comment:** This clocked gate has a built-in implementation and thus there is no need to implement it.

Figure 3.1: API for a *data flip-flop* gate; c.f. Nand gate regarding primitive nature.

 **Registers** a storage device that can “remember” a value over time:  $out(t) = out(t-1)$ ; note, a DFF can only output its previous input (i.e.  $out(t) = in(t-1)$ ).



 **Chip name:** Bit  
**Inputs:** in, load  
**Outputs:** out  
**Function:** If  $load(t-1)$  then  $out(t) = in(t-1)$   
 else  $out(t) = out(t-1)$




**Chip name:** Register  
**Inputs:** in[16], load  
**Outputs:** out[16]  
**Function:** If  $load(t-1)$  then  $out(t) = in(t-1)$   
 else  $out(t) = out(t-1)$   
**Comment:** “=” is a 16-bit operation.

Figure 3.2: Top: API for a single-bit register (a *Bit*, or *binary cell*) chip.


Bottom: API for a 16-bit register: to **read**, we identify the output; to **write**, we write a new data value  $in = d$  into the register and assert (set to 1) the *load* input, and in the next clock cycle the register commits to the new data (outputting  $d$ ).

 *Notation 3.2.* Represent the clock signal of a sequential chip:



 *Remark (WARNING:).* The following 1-bit register description from a DFF is invalid:





It is not clear how we'll never load new data into this because should we draw input from the *in* or *out* wire? More generally, chips design dictates that *internal pins must have a fan-in of 1*.

Once we have the mechanism for remembering a single bit with time, we construct  $n$ -bit wide registers by forming an array of as many single-bit registers as needed.

 


Figure 3.4: From single-bit to multi-bit registers.

The *width* of a register is the number of bits it holds (e.g. 16,32,64, ...).

The multi-bit contents of a register are the *words*.

**Memories** Stacking many register form a *Random Access Memory (RAM)* unit; this name is derived from the requirement that read/write operations of any randomly chosen word on RAM should be accessed directly (in equal speed, irrespective of its physical location). Hence, a classical RAM device accepts three inputs: *data*, *address*, and *load*. *Address* specifies which RAM register to access in the current time unit. If  $load = 0$  (a read operation) the RAM's  $out = value\ of\ selected\ register$ ; otherwise (a write operation,  $load = 1$ ) the selected memory register commits to the input value.


 


Figure 3.5: RAM.

 The *width* of RAM of one of its registers (32- or 64-bit wide RAM).  
 The *size* of RAM is the number of registers in the RAM.



**Chip name:** RAMn // n and k are listed below

**Inputs:** in[16], address[k], load

**Outputs:** out[16]

**Function:** out(t)=RAM[ address(t) ](t)  
 If load(t-1) then  
     RAM[address(t-1)](t)=in(t-1)

**Comment:** "=" is a 16-bit operation.

**The specific RAM chips needed for the Hack platform are:**

Chip name	n	k
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14

Figure 3.6: API for 16-bits wide RAM with various sizes (RAM8, RAM64, RAM512, RAM4K and RAM16”).

*Read:* to read register number  $m$ , input  $address = m$  outputting the value of this register (combinational operation independent of the clock).

*Write:* to write new data  $d$  to register number  $m$ , input  $address = m, in = d$  and assert the *load* input. In the next clock cycle, the selected register commits the new value  $d$ , as well as the RAM outputting this.

**Counters** a sequential chip whose state is  $c \in \mathbb{Z}$  (typically 1) that increments every time unit, effecting  $out(t) = out(t-1) + c$ . Use for tasks that require such a measure.

### 3.2 Specification [p47]

#### Hierarchy of sequential chips:

- Data Flip-flops (DFFs).
- Registers (based on DFFs).
- Memory banks (based on registers).
- Coutner chips (based on registers).

### 3.3 Implementation [p50]

### 3.4 Perspective [p52]

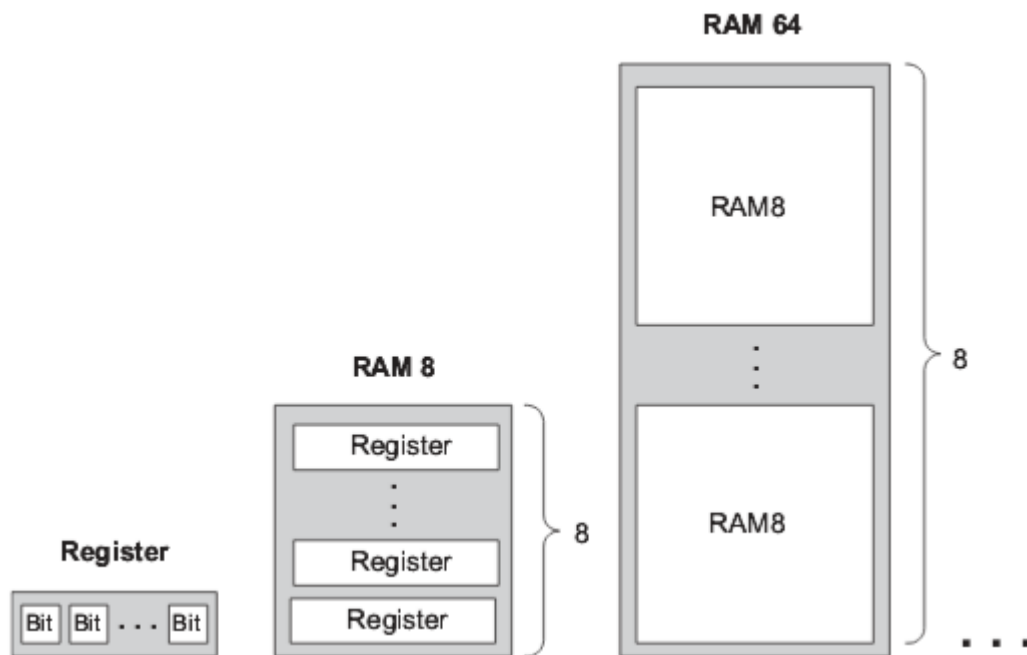


Figure 3.8: Construction of memory banks by recursive ascent.

## 4 Machine Language [p57]

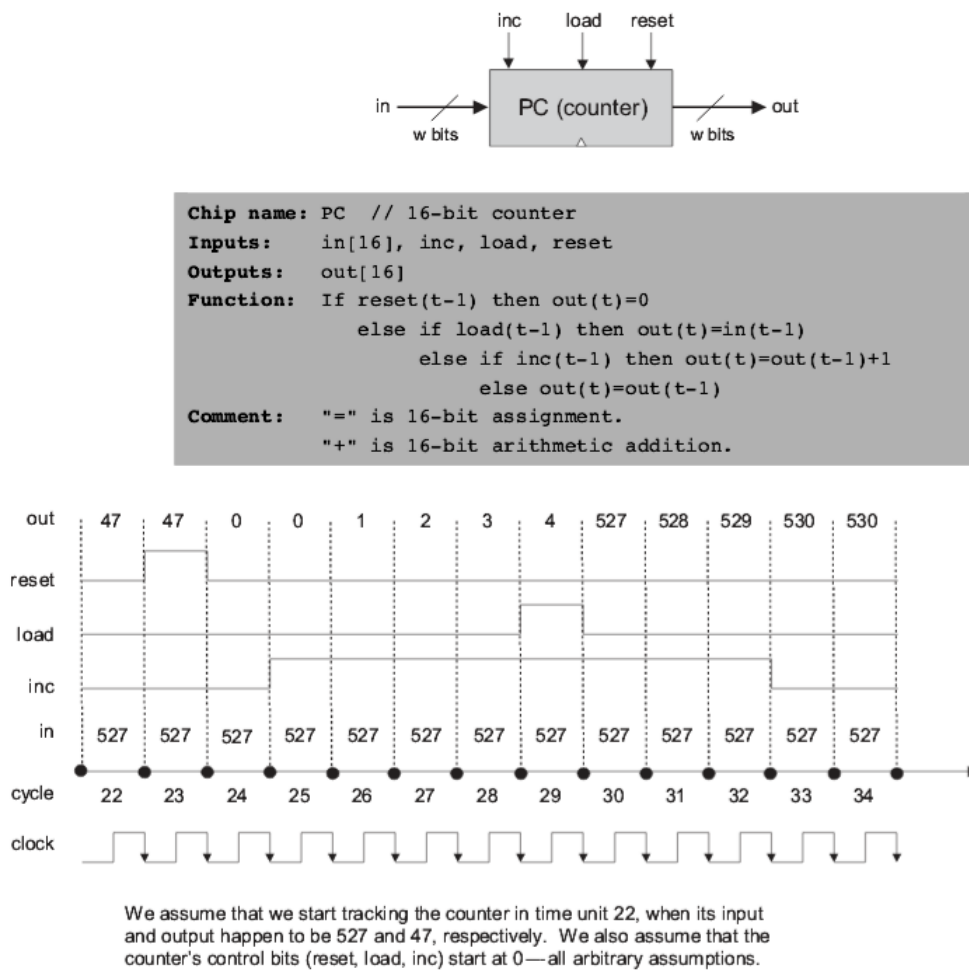


Figure 3.7: API for a counter chip; similar to register with two extra inputs:

*inc* = 1  $\Rightarrow$  increment the counter's state every clock cycle, outputting the result.

*reset* = 1  $\Rightarrow$  reset counter to 0.